

Seat No. **OCT-NOV 2025 WINTER EXAMINATION****12609 Bachelor of Technology (NEP-2.1)****Sub. Name: Basic Electrical Engineering****Sub. Code: 114850****Day and Date: Friday ,23-01-2026****Total Marks: 60****Time: 10:30 AM To 12:30 PM****Instructions: 1. Use of Scientific calculator is allowed****Special Inst.: 1. Question No.:-1 is compulsory.****2. Attempt any THREE questions from Question No. 2 to 5****Q1) Solve following MCQ.****[6]**

- i. Kirchoff's Current Law (KCL) is based on the principle of conservation of
- A. Energy
  - B. Charge
  - C. Momentum
  - D. Mass
- ii. Magnetic Flux Density (B) is defined as:
- A. Flux per unit area ( $B = \Phi/A$ )
  - B. MMF per unit length
  - C. Total magnetic lines
  - D. Strength of the magnet
- iii. The Form Factor of a pure sinusoidal waveform is:
- A. 1.0
  - B. 1.414
  - C. 1.11
  - D. 0.707
- iv. What is the phase displacement between the three phases in a 3-phase supply?
- A. 90 degrees
  - B. 180 degrees
  - C. 120 degrees
  - D. 60 degrees
- v. The core of a transformer is laminated to reduce:
- A. Hysteresis Loss
  - B. Eddy Current Loss
  - C. Copper Loss
  - D. Friction Loss

- vi. ELCB stands for: A. Electrical Line Circuit Breaker  
A. Electrical Line Circuit Breaker  
B. Earth Leakage Circuit Breaker  
C. Earth Line Current Breaker  
D. Emergency Load Control Breaker

**Q2) Answer the following questions [18]**

- a. Define the terms in DC- E.M.F, Potential Difference, Current, Resistance. [6]
- b. Two batteries A & B are connected in parallel to supply a load resistance of 10 ohms. Battery A has an EMF of 50V with an internal resistance of 1 ohm & battery B has an EMF of 70V with an internal resistance of 1 ohm. Determine the current delivered by each battery & current in the load resistance. Also calculate power supplied to 10 ohm resistance. Use Node analysis. [6]
- c. Distinguish between Electric & Magnetic circuit. [6]

**Q3) Answer the following questions. [18]**

- a. Define- i) Form Factor ii) Peak factor iii) Average Value iv) RMS Value [6]
- b. Explain three phase Star & Delta connections with their line & phase quantities. [6]
- c. A R-L series is connected across 250 volts, 50 Hz AC supply, Draws a current of 10 A at 0.8 lagging power factor. Find- (i) Impedance (ii) Resistance (iii) Inductance. [6]

**Q4) Answer the following questions. [18]**

- a. Explain construction & working principle of single phase transformer. [6]
- b. Comment on MCB & ELCB. Also state its advantages, disadvantages and applications. [6]
- c. A 30 KVA 3300/230 Volt single phase 50 Hz transformer has full load copper loss 500 watts & iron loss 300 watts. Calculate transformer efficiency at full load & also at half load, when power factor is 0.866 lagging. [6]

**Q5) Answer the following questions. [18]**

- a. Explain how single-phase sinusoidal voltage is generated in AC. [6]
- b. Derive the mathematical expression for RMS value of sinusoidal AC by analytical method. [6]
- c. Write a short note on Domestic energy bill. [6]

## **End Of Question Paper**

**Important Note for Chief Exam Officer / SRPD Coordinator / Sr Supervisor/ Student -**

This Question Paper may be distributed for following Subjects as common code.

सदरची प्रश्नपत्रिका खालील विषयांकरिता वितरित करता येईल.

- 1] (12609) Bachelor of Technology (NEP-2.1) (114850) Basic Electrical Engineering Part 1 SEM 1

516628