

|          |
|----------|
| Seat No. |
|----------|

**OCT-NOV 2025 WINTER EXAMINATION****11731 Bachelor of Technology (NEP-2.0)****Sub. Name: Basic Electrical Engineering****Sub. Code: 108720****Day and Date: Friday ,23-01-2026****Total Marks: 60****Time: 10:30 AM To 01:00 PM**

- Instructions:**
1. All questions are compulsory
  2. Draw neat labelled diagrams wherever necessary
  3. Figures to the right indicate full marks
  4. Use of Scientific calculator is allowed

**Q1)** Attempt any THREE of the following **[15]**

- a. Two batteries A & B are connected in parallel across a load resistance of 4 ohm. The emf & internal resistance of battery A & B are 20 volts, 2 ohm and 24 volts, 4 ohm respectively, using mesh or node analysis, Find (i) current in battery A,  
ii. current in battery B  
iii. current in load resistance. **[5]**
- b. Explain the concept of magnetic leakage & fringing in magnetic circuits. **[5]**
- c. Derive the expression for RMS value of sinusoidal AC by analytical method. **[5]**
- d. State and explain KCL & KVL. **[5]**

**Q2)** Attempt any THREE of the following. **[15]**

- a. State the advantages of three phase supply system over single phase supply system. **[5]**
- b. Prove that line voltage is  $\sqrt{3}$  times phase voltage in a three phase balanced star connected system. **[5]**
- c. Draw the 3 phase star connection and show all the line & phase quantities. **[5]**
- d. Define line voltage, line current, phase voltage & phase current in a three phase system. **[5]**

**Q3)** Attempt the following **[15]**

- a. A 30 KVA 3300/230 Volt single phase 50 Hz transformer has full load copper loss 500 watts & iron loss 300 watts. Calculate transformer efficiency at full load & also at half load, when power factor is 0.866 lagging. **[8]**

- b.** Draw & explain Capacitor split phase induction motor. State applications. [7]  
OR  
Explain construction & working principle of single-phase transformer.

**Q4)** Attempt any THREE of the following. [15]

- a.** State Necessity of Earthing & Explain any one in detail with neat sketch. [5]  
**b.** Compare Fuse and MCB on various aspects. [5]  
**c.** Describe operating principle of LED Lamp. State different types of LED's. [5]  
**d.** Comment on different types of batteries with its characteristics. [5]

## **End Of Question Paper**

**Important Note for Chief Exam Officer / SRPD Coordinator / Sr Supervisor/ Student -**

This Question Paper may be distributed for following Subjects as common code.

सदरची प्रश्नपत्रिका खालील विषयांकरिता वितरित करता येईल.

- 1] (11731) Bachelor of Technology (NEP-2.0) (108720) Basic Electrical Engineering Part 1 SEM 1